

Description

The STR-X6700 series are power ICs for switching power supplies, incorporating a power MOSFET and a quasi-resonant controller IC.

Including an auto standby function in the controller, the product achieves the low standby power by the automatic switching between the quasi-resonant operation in normal operation, the bottom-skip operation under medium to light load conditions and the burst-oscillation under light load conditions.

The products are supplied in a seven-pin fully-molded TO3P style package, and achieve high cost-performance power supply systems with few external components.

Features

- Current Mode Quasi-Resonant Control
- Multi-mode Control

The optimum operation depending on load conditions is changed automatically and is achieved high efficiency operation across the full range of loads.

Operation Mode

Normal load ----- Quasi-resonant


Medium to light load ----- One bottom-skip

Light load -----

Intermittent operation by UVLO or burst oscillation


- Built in PWM Oscillator (To reduce the products stress in startup and short cuecuit mode, the IC opetares in PWM (about 22 kHz) until the quasi-resonant operation is established)
- Soft-start Function
- Step-drive Function
- Limmiting the Maximum On-time
- Adjustable OCP Operation Point for Input Voltage
- Protections
Overcurrent Protection (OCP): Pulse-by-Pulse
Overload Protection (OLP): Latched Shutdown
Overvoltage Protection (OVP): Latched Shutdown

Typical Application

 

Packages

TO3P-7L

 

Not to scale

Selection Guide

Part Number	Medium to Light load Operation	Light Load Operation
STR-X67xxB	—	Intermittent operation by UVLO
STR-X67xx	One bottom-skip	Auto burst
STR-X6729 STR-X67xxN STR-X67xxM	One bottom-skip	Intermittent operation by UVLO
STR-X67xxF	—	Auto burst

Specifications

Part Number	V _{DSS} (min.)	R _{DS(ON)} (max.)	P _{OUT} (Open frame) ⁽¹⁾	
			230VAC	85 to 265VAC
STR-X6729	450 V	0.189 Ω	280 W ⁽²⁾	360 W ⁽³⁾
STR-X6737 STR-X6737M	500 V	0.36 Ω	220 W ⁽²⁾	290 W ⁽³⁾
STR-X6759N STR-X6759B STR-X6759F	650 V	0.385 Ω	210 W ⁽²⁾	280 W ⁽³⁾
STR-X6757 STR-X6757N		0.62 Ω	320 W	210 W
STR-X6750B STR-X6750F		0.62 Ω	320 W	210 W
STR-X6756		0.73 Ω	300 W	180 W
STR-X6769 STR-X6769B	800 V	0.66 Ω	310 W	200 W
STR-X6768N		1.0 Ω	200 W	130 W

⁽¹⁾ The output power is actual continues power that is measured at 50 °C ambient. The peak output power can be 120 to 140 % of the value stated here. Core size, ON Duty, and thermal design affect the output power. It may be less than the value stated here.

⁽²⁾ 100VAC

⁽³⁾ 210VAC

Applications

- White Goods
- Office Automation Equipment
- Industrial Equipment

Contents

Description	1
Contents	2
1. Operational Description	3
1.1. Startup Operation	3
1.2. Constant Output Voltage Control	4
1.3. Soft Start Function	5
1.4. Quasi-Resonant Operation	5
1.5. Bottom Skip Quasi-resonant Operation	7
1.6. Standby Modes	9
1.6.1. UVLO Intermittent Oscillation Operation	9
1.6.2. Automatic Burst Oscillation Operation	11
1.7. Step-drive Function	11
1.8. Maximum On-Time Limitation Function	11
1.9. Latch Circuit	11
1.10. Overvoltage Protection (OVP)	12
1.11. Overload Protection (OLP)	12
1.12. Overcurrent Protection (OCP)	14
2. Design Notes	15
2.1. External Components	15
2.2. Transformer Design	16
2.3. PCB Trace Layout and Component Placement	18
Important Notes	19

Not Recommended for New Designs

1. Operational Description

Unless otherwise specified, the electrical characteristics values of STR-X6756 are used in this section.

1.1. Startup Operation

Figure 1-1 shows the VCC pin peripheral circuit.

The startup circuit detects the VCC pin voltage, and makes the control IC start and stop operation. At startup, C2 is charged through a startup resistor R1. When the VCC pin voltage reaches to $V_{CC(ON)} = 18.2\text{ V}$ (typ.), the IC starts operation.

The R1 value needs to be set for more than the hold current of the latch circuit ($I_{CC(H)} = 140\ \mu\text{A}$ max.) in the minimum AC input condition.

If the value of R1 is too high, the startup time (C2 charge time) becomes long. Thus, R1 should be set to consider with C2 value.

In general SMPS specification, the value of C2 and R2 are set as follows:

C2 is 4.7 μF to 47 μF ,

R2 is 47 k Ω to 150 k Ω for 100VAC or universal AC input, and 82 k Ω to 330 k Ω for 230VAC input.

 


Figure 1-1. VCC Pin Peripheral Circuit

Figure 1-2 shows the relationship between the VCC pin current and the VCC pin voltage.

When the VCC pin voltage reaches to $V_{CC(ON)} = 18.2\text{ V}$ (typ.), the IC starts operation and the circuit current is increases. When the VCC pin voltage decreases to $V_{CC(OFF)} = 9.7\text{ V}$ (typ.), the UVLO circuit operates to stop the control circuit, and the IC returns to its initial state.

After the control circuit starts its operation, the rectifying and smoothing voltage of the auxiliary winding, D, is supplied to the VCC pin.

In the specification of input and output voltage variation of power supply, the number of turns of the auxiliary winding should be set so that the VCC pin voltage becomes within following range.

$$V_{CC(OFF)\text{ max.}} < V_{CC} < V_{CC(OVP)\text{ min.}}$$

$$\rightarrow 10.6\text{ V} < V_{CC} < 25.5\text{V}$$

The voltage of the auxiliary winding is recommended about 18 V.

 


Figure 1-2. VCC Pin Current versus Voltage

 


Figure 1-3. VCC Pin Voltage instartup

Figure 1-3 shows the startup voltage waveform of the VCC pin.

The auxiliary winding voltage does not immediately increase up to the set voltage after the control circuit starts its operation. That is why the VCC pin voltage starts dropping. The Operation-Stop voltage, $V_{CC(OFF)}$, is set as low as 10.6 V (max.), the auxiliary winding voltage reaches a stabilized voltage before it drops to $V_{CC(OFF)}$, and the control circuit continues its operation.

If the VCC pin voltage decrease to $V_{CC(OFF)}$, the startup failure is cased as shown in Figure 1-3. In the case, increase the value of C2 and check the startup time in actual operation.

In actual power supply circuits, there are cases in which the VCC pin voltage fluctuates in proportion to the output current, I_{OUT} (see Figure 1-4), and the Overvoltage Protection function (OVP) on the VCC pin

may be activated. This happens because C2 is charged to a peak voltage on the auxiliary winding D, which is caused by the transient surge voltage coupled from the primary winding when the power MOSFET turns off.

For alleviating C2 peak charging, it is effective to add some value R2, of several tenths of ohms to several ohms, in series with D1 (see Figure 1-5).

The optimal value of R2 should be determined using a transformer matching what will be used in the actual application, because the variation of the auxiliary winding voltage is affected by the transformer structural design.

Furthermore, the variation ratio of the VCC pin voltage becomes worse due to a loose coupling between primary and secondary windings of the transformer (the coupling between the auxiliary winding and the stabilized output winding for the constant voltage control). Therefore, when designing a transformer, the winding position of the auxiliary winding needs to be studied carefully.

 


Figure 1-4. Variation of VCC pin Voltage and Output Current

 


Figure 1-5. VCC Peripheral Circuit

1.2. Constant Output Voltage Control

Figure 1-6 shows the constant output voltage control circuit, Figure 1-7 shows the waveforms of constant output voltage control mode at no quasi-resonant control signal.

The IC achieves the constant voltage control of the power supply output by using the current-mode control method, which enhances the response speed and provides the stable operation.

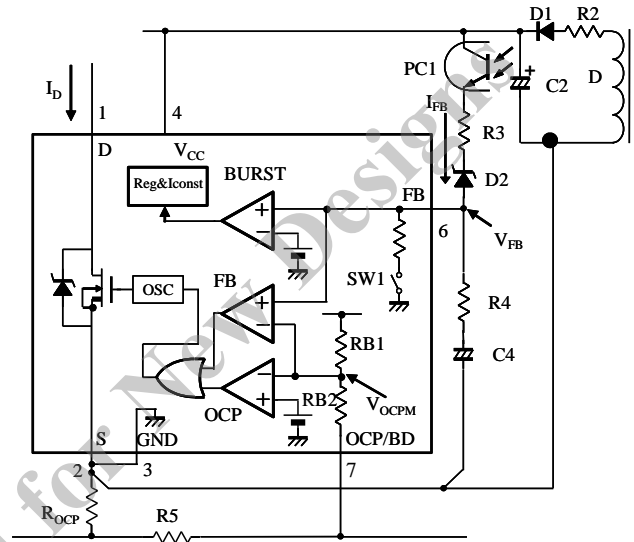


Figure 1-6. Constant Output Voltage Control Circuit

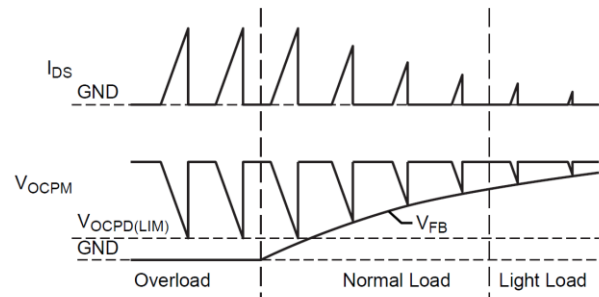


Figure 1-7. Constant-voltage control at fixed oscillation frequency (quasiresonant signal not available)

As shown in Figure 1-6, the peak value of the power MOSFET drain current is changed by comparing the FB pin voltage with the internal V_{OCPM}.

A control signal from an error amplifier (FB current) is fed into the FB pin through the optocoupler, PC1.

The input FB current is transformed into feedback voltage, V_{FB}, by the internal resistor (SW1 is turned on during normal status).

Drain current, I_D, is detected as negative signal by detection current, R_{OCP}. This signal is divided by the

internal resistor (RB1 and RB2) to make V_{OCPM} .

V_{FB} and V_{OCPMFB} input to the FB comparator, and the current mode that controls drain peak current is controlled by it.

In the period of overload in Figure 1-7, V_{OCPM} decreases. When V_{OCPM} decreases to $V_{COPBD(LIM)} = -0.94$ V (typ.), the overcurrent protection is activated, and limits the drain current.

In the period from normal load to light load in Figure 1-73, the drain current decreases because the FB current increases and V_{FB} rises.

When V_{FB} exceeds the FB pin threshold voltage $V_{FB(OFF)} = 1.45$ V (typ.) at light load, the IC operates in burst oscillation so as not to raise the secondary-side output voltage.

The Zener diode, D2, has $V_Z = 5.6$ to 6.2 V, and is connected in series with the optocoupler for the countermeasure against the overvoltage of FB pin. The FB pin voltage must not rise over 9 V in the dynamic load fluctuation and the standby operation that is the intermittent operation by UVLO.

R3 value is about 1 kΩ.

About R5 value setting, see Section 1.12.

1.3. Soft Start Function

Figure 1-8 shows an example of the waveform pattern at soft start operation.

At the power supply startup, the soft start operation charging current, $I_{SSOLP(SS)} = -550$ μA (typ.), flows and charges C3 of SS/OLP pin to the soft start operation stop voltage, $V_{SSOLP(SS)} = 1.2$ V (typ.). This period is the soft start period. By comparing the oscillation waveforms of the SS/OLP pin and that of the internal control, the soft-start widening of the on-width is activated, resulting in the reduction of the stress of voltage and current of the power MOSFET and the secondary diode.

In addition, the soft-start is operated every time in the burst oscillation. Gradual increase of drain current suppresses audible noise from the transformer.

Table 1-1, Soft Start Reference Time
(Calculated value: Charging current -550 μA (typ.))

Capacitance of C_{SS}	Soft Start Time
0.47 μF	1.0 ms
1 μF	2.2 ms
2.2 μF	4.8 ms
3.3 μF	7.2 ms
4.7 μF	10.3 ms

 


Figure 1-8. Soft Start Operation

1.4. Quasi-Resonant Operation

The quasi-resonant operation reduces the switching loss and noise, and achieves the high-efficiency and low-noise power supply. The IC operates in quasi-resonance at one-bottom-skip operation.

Figure 1-9 shows the flyback type circuit. The meaning of symbols in Figure 1-9 are shown in Table 1-2.

Flyback circuit is the method to supply the energy stored in the transformer when the power MOSFET turns off.

In flyback, the power MOSFET remains off after turning off and releasing the energy to the secondary side. At this time, the V_{DS} freely oscillates in the frequency determined by L_P and C_V .

The quasi-resonant operation turns on the power MOSFET at the bottom of V_{DS} voltage waveform in the free oscillation period. (bottom-on operation)

Figure 1-10 shows the V_{DS} voltage waveform at the ideal bottom-on operation.

When the delay time between the start of V_{DS} voltage waveform of free oscillation and the turning off the power MOSFET is t_{ONDLY} , the t_{ONDLY} at the ideal bottom-on operation is in the half-cycle of the free oscillation, and calculated by the following equation.

$$t_{ONDLY} \doteq \pi \sqrt{L_P \times C_V} \quad (1)$$

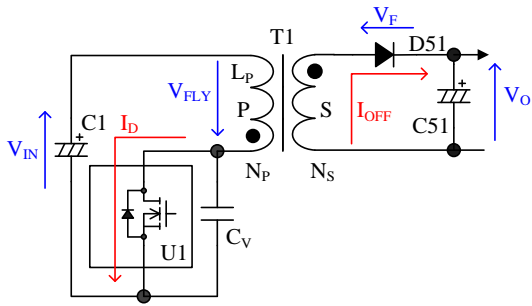


Figure 1-9. Basic Flyback Converter Circuit

Table 1-2. Meaning of Symbols (Figure 1-9)

Symbol	Meaning
V_{IN}	Input voltage
V_{FLY}	Flyback voltage, $V_{FLY} = \frac{N_P}{N_S} \times (V_O + V_F)$
V_{DS}	The voltage between drain and source of the power MOSFET
N_P	The number of turns in the primary side
N_S	The number of turns in the secondary side
V_O	Output voltage
V_F	The forward voltage drop of secondary rectifier diode
I_D	Drain current of the power MOSFET
I_{OFF}	The current that flows through the secondary rectifier diode when the power MOSFET is in off state.
C_V	Voltage resonant capacitor
L_P	Primary inductance

 


Figure 1-10. Ideal Bottom-on Operation Waveform

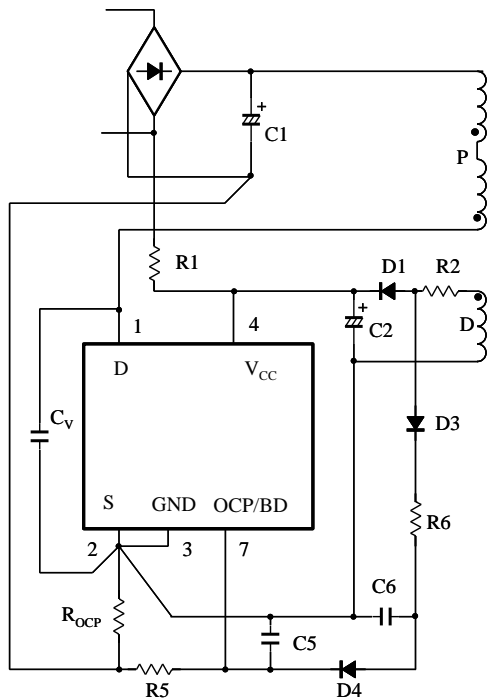


Figure 1-11. Quasi-resonance and Delay Circuit

The delay circuit is configured by the auxiliary winding D, and D3, D4, C6, and R6 between OCP/BD pin in Figure 1-11.

When the OCP/BD pin voltage exceeds the quasi-resonant operation threshold voltage 2, $V_{OCP(TH2)} = 0.8$ V (typ.), by the auxiliary winding after the power MOSFET turns off, the power MOSFET remains off until the OCP/BD pin voltage decreases to the quasi-resonant operation threshold voltage1, $V_{OCPBD(TH1)} = 0.4$ V (typ.).

When the transformer energy release is finished, the auxiliary winding voltage starts to decrease and the C6 voltage is discharged through R5. When the OCP/BD pin voltage decreases to the quasi-resonant operation threshold voltage, $V_{OCPBD(TH1)} = 0.4$ V (typ.), or less, the power MOSFET turns on. This discharge period is the delay time. The delay time needs to be set by adjusting C6, monitoring the operating waveform, so that the power MOSFET turns on when the V_{DS} of the power MOSFET hits the lowest point. The malfunction of quasi-resonant operation is prevented by the voltage difference between $V_{OCPBD(TH1)}$ and $V_{OCP(TH2)}$.

At the power supply startup or at low bias winding voltage due to a winding short, if the OCP/BD pin voltage after turning on is not $V_{OCPBD(TH2)} = 0.8$ V (typ.) or higher, the PWM operation of fixed oscillation frequency, 22 kHz (typ.), is activated with the internal oscillator, and the stress of voltage and current of the power MOSFET and the secondary diode is reduced.

In setting R6, the OCP/BD pin voltage needs to be the

absolute maximum rating applied voltage of 5 V (max.) or less. In a normal condition, it should be approximately 1.5 V. The resistance of R_{OCP} is small enough to be ruled out. When the auxiliary winding voltage is 18 V, the R6 that the OCP/BD pin voltage is 1.5 V is to be about 1 k Ω to 3.3 k Ω . The delay time depends on the C6 capacitance. When the delay time is 2.2 μ s, the R5 and C6 are temporarily set at 1.5 k Ω and 1000 pF, respectively. The constant is adjusted so that the waveform of OCP/BD pin voltage is the bottom-on, monitoring the OCP/BD pin voltage in actual operation.

For the setting of R5 and C5, see Section 1.12 Overcurrent Protection (OCP).

When the constant is adjusted, if the turn-on timing does not match the bottom of V_{DS} , the turn-on should be set earlier than the bottom point as shown in Figure 1-12 so that the operation becomes stable.

 


Figure 1-12. Bottom-on Setting

1.5. Bottom-skip Quasi-resonant Operation

In addition to the quasi-resonant operation in the previous section, the IC incorporates a bottom-skip mode in order to suppress the increase of oscillating frequency during a light-to-medium load. The bottom-skip quasi-resonant operation is incorporated in the STR-X67xx, STR-X6729, STR-X67xxN and the STR-X67xxM.

Bottom-skip quasi-resonance is operated as follows:

Secondary load status is monitored by the OCP/BD pin voltage that is similar to the waveform of drain current, I_D . The load status is compared to the internal BSD comparator. The operation is shifted to quasi-resonant operation at heavy load, and shifted to bottom-skip quasi-resonant operation at light-to-medium load.

Figure 1-13 shows the timing of shift from quasi-resonant to bottom-skip quasi-resonant.

 


Figure 1-13. Quasi-resonant to Bottom-skip Operation Timing

In the following descriptions of mode shift operation, the OCP/BD pin gate falling voltage of the power MOSFET is V_{OCP} .

- Quasi-resonant operation \Rightarrow bottom-skip mode

Quasi-resonance is operated under the following condition:

$$|V_{OCP}| > |V_{OCPBD(BS2)}|$$

When the load becomes lighter, the I_D becomes smaller. As a result, when V_{OCP} is higher than $V_{OCPBD(BS2)}$, the operation is shifted to bottom-skip mode, and the threshold is automatically changed to $V_{OCPBD(BS1)}$. The falling edges (OCP/BD pin voltage is less than $V_{OCPBD(TH1)}$ due to the free oscillation of V_{DS}) of quasi-resonant signal is counted in the IC, and the one-cycle free oscillation is skipped, resulting in the reduction of the switching loss.

- Bottom-skip mode \Rightarrow quasi-resonant operation

Bottom-skip mode is operated under the following condition:

$$|V_{OCP}| < |V_{OCPBD(BS1)}|$$

When the load becomes lighter, the I_D becomes larger. As a result, when V_{OCP} is higher than $V_{OCPBD(BS1)}$, the

operation is shifted to quasi-resonant operation, and the threshold is automatically changed to $V_{OCPBD(BS2)}$.

As shown in Figure 1-14, in the process of load current increase or the load current decrease, hysteresis is set to make the switching waveform stable around the shift threshold, resulting in a stable operation mode shift.

 


Figure 1-14. Hysteresis at Operation Mode Shift

1.6. Standby Modes

The STR-X6700 series have two types of standby modes. See the product lineup for the relationship between products and standby modes.

1.6.1. UVLO Intermittent Oscillation Operation

The switch is provided to the detection circuit of the secondary output so that the circuit is switched to control the auxiliary winding voltage to be $V_{CC(OFF)}$ or lower. This decreases the output voltage at standby of remote control, and switches to the UVLO intermittent oscillation operation to reduce the power consumption.

Figure 1-15 shows the secondary circuit example in UVLO intermittent oscillation. When the standby signal is input to the secondary side, and the switch, SW, turns on, the auxiliary winding voltage decreases according to the decrease of the output voltage. The IC stops operation when the VCC pin voltage is the operation – stop voltage, $V_{CC(OFF)} = 9.7 \text{ V}$ (typ.), or lower. Then, C2 is charged through the startup resistor, R1, and the VCC pin voltage increases again. When the VCC pin voltage reaches the operation-start voltage, $V_{CC(ON)} = 18.2 \text{ V}$ (typ.), the IC starts operation again. However, the VCC pin voltage switches to the UVLO intermittent oscillation operation that repeats between $V_{CC(ON)}$ and $V_{CC(OFF)}$ since the auxiliary winding voltage is $V_{CC(OFF)}$ or lower. Therefore, the energy is supplied to the secondary side only for a short switching period that the VCC pin decreases to $V_{CC(OFF)}$ from $V_{CC(ON)}$.

Figure 1-16 shows the timing chart at operation shift.

When the UVLO intermittent oscillation frequency is in a human audible range (20 Hz to 20 kHz), the audible noise of transformer may occur.

As a measure against the audible noise, the switching current can be suppressed by decreasing the startup resistor, R1, and shortening the intermittent oscillation frequency, however, the R1 loss increases. Therefore, in order to increase the intermittent frequency and suppress the switching current, the STR-X6700 series

incorporates the function that decreases the difference between $V_{CC(OFF)}$ and the operation-start power voltage to about 1/5 of the difference in normal operation by decreasing the operation-start voltage to the operation-start voltage at standby, $V_{CC(S)} = 11.1 \text{ V}$ (typ.), when the FB pin voltage reaches the standby operation threshold voltage, $V_{FB(S)} = 1.1 \text{ V}$, or higher.

Because the oscillation stops during the period of shift to UVLO intermittent operation from normal operation, the output voltage continues to decrease. Therefore, the load should be set to keep the voltage higher than the required voltage by the secondary output voltage.

Because the oscillation stops during the period of shift to normal operation from standby operation, the output voltage continues to decrease until the VCC pin voltage reaches $V_{CC(ON)} = 18.2 \text{ V}$ (typ.). Therefore, the load should be set to keep the voltage higher than the required voltage by the secondary output voltage until the normal oscillation starts.

The sequence of load shift is necessary in the device during the operation shift period.

Taking the operational mechanism into consideration, the standby operation by UVLO intermittent oscillation is in a minute load region of about several decades of mW to 0.2 W at maximum.

When the output ripple voltage or the voltage fluctuation except the stabilized output lines is too high, or the audible noise of transformer occurs, it is required to consider increasing the capacitance of output smoothing capacitor.

For the audible noise of transformer, please contact transformer manufacturers as there are measures such as ferrite core adhesion and varnish impregnation.

Though the minimum on-time, $t_{ON(MIN)}$, is set in the IC, the products that operate by UVLO intermittent oscillation at light load release the limit of the minimum on-time, $t_{ON(MIN)}$, at quasi-resonant operation to operate to zero. When the oscillation frequency at light load increases and the switching loss increases, please pay attention to temperature rise.

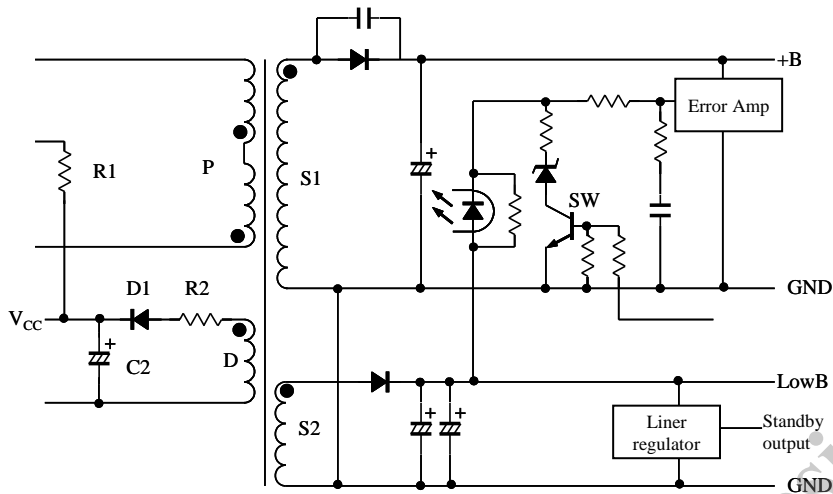


Figure 1-15. Secondary Circuit Example of UVLO Intermittent Oscillation

 


Figure 1-16. Timing Chart at Operation Shift

1.6.2. Automatic Burst Oscillation Operation

The minimum on-time, $t_{ON(MIN)}$, is set internally. When the load becomes lighter and the time width of drain current, I_D reaches $t_{ON(MIN)}$, the feedback current increases to increase the FB pin voltage. When the FB pin voltage reaches the FB pin threshold voltage, $V_{FB(OFF)} = 1.45 \text{ V}$, the oscillation operation stops. When the FB pin voltage decreases, the oscillation operation is automatically started (automatic burst oscillation operation). This reduces the switching loss and improves the efficiency at standby.

1.7. Step-drive Function

The drive circuit of the power MOSFET incorporates the step-drive circuit and reduces noise at turn on.

As shown in Figure 1-17, when the internal power MOSFET turns on, Tr1 turns on and the gate voltage gradually increases by the drive current limited by RG1. Tr2 turns on after about $0.9 \mu\text{s}$ and the high current limited by RG1 and RG2 flows. This increases the gate voltage rapidly. When the internal power MOSFET turns off, Tr1 and Tr2 turns off, and Tr3 turns on. The gate charge of the power MOSFET is rapidly discharged through the RG3 of low resistance.

The drive voltage is supplied by the constant voltage source, $V_{DRV} = 7.5 \text{ V}$ (typ.), and not affected by VCC pin voltage.

Step drive function suppresses surges of drain current by switching the gate voltage at power MOSFET turn on in two steps, and then supplies the enough gate voltage.

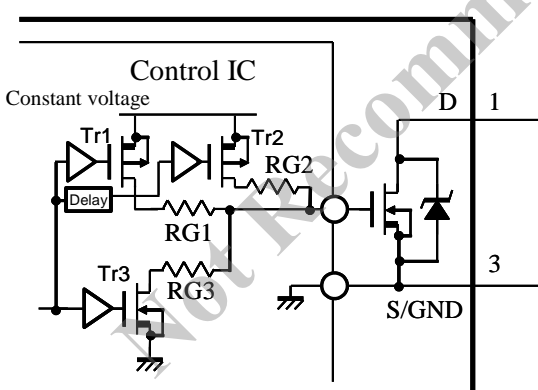


Figure 1-17. Step Drive Circuit

1.8. Maximum On-time Limitation Function

When the input voltage is low or in a transient state such that the input voltage turns on or off, the on-time of the incorporated power MOSFET is limited to the maximum on-time, $t_{ON(MAX)} = 32.5 \mu\text{s}$ in order to prevent

the decrease of switching frequency. Thus, the audible noise of the transformer at power supply on / off is suppressed.

In designing a power supply, the on-time of the power MOSFET must be less than $t_{ON(MAX)}$ under the condition of the minimum input voltage and the maximum output power (see Figure 1-18).

If such a transformer is used that the on-time is $t_{ON(MAX)}$ or more, under the condition of the minimum input voltage and the maximum output power, the on-time of the power MOSFET is limited at the maximum on-time. Therefore, the output power may be the specified output power or lower at the lower limit of the input voltage. In that case, the transformer should be redesigned considering the followings:

Inductance, L_p , of the transformer should be lowered in order to raise the switching frequency.

Lower the primary and the secondary turns ratio, N_p / N_s , to lower the duty cycle.

 


Figure 1-18. Confirmation of Maximum On-time

1.9. Latch Circuit

Latch circuit stops the oscillation operation in latch mode in the operation of OVP (Overvoltage Protection) and OLP (Overload Protection).

When the latch circuit operates and stops the oscillation operation, the VCC pin voltage starts to decrease. When the voltage decreases to the operation-stop voltage, $V_{CC(OFF)} = 9.7 \text{ V}$ (typ.), the circuit current of IC decreases. Then, the VCC pin voltage starts to increase by the current supply from the startup resistor, R1. When the VCC pin voltage reaches the operation-start voltage, $V_{CC(ON)} = 18.2 \text{ V}$ (typ.), the circuit current increases again. VCC pin voltage repeats increasing / decreasing between $V_{CC(ON)}$ and $V_{CC(OFF)}$, as shown in Figure 1-19.

The startup resistor, R1, is set so that the latch circuit holding current, $I_{CC(H)} = 140 \mu\text{A}$ (max), or higher flows at the lower limit of AC input voltage.

Turning off the AC input and decreasing the VCC pin voltage to the latch circuit releasing voltage, $V_{CC(La,OFF)} = 7.2 \text{ V}$ (typ.) releases the latch mode.

 


Figure 1-19. V_{CC} Pin Voltage Waveform at Latch Mode

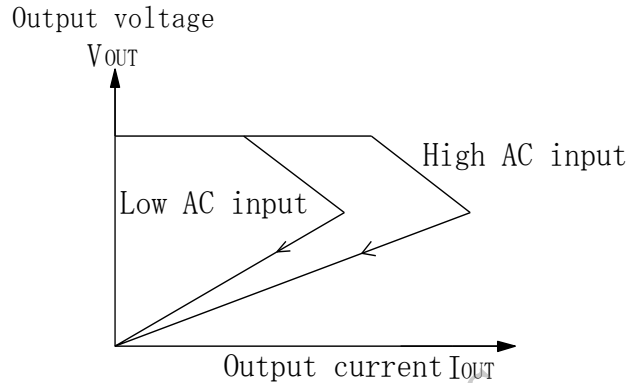


Figure 1-20. Output Overload Characteristics

1.10. Overvoltage Protection (OVP)

When a voltage between VCC pin and GND pin increases to V_{CC(OVP)} = 27.7 V or higher, the Overvoltage Protection (OVP) is activated, and the IC stops switching operation at the latched mode.

When the VCC pin voltage is provided by using auxiliary winding of transformer, the overvoltage conditions such as output voltage detection circuit open can be detected because the VCC pin voltage is proportional to the output voltage. The approximate value of the output voltage, V_{OUT(OVP)}, in OVP is calculated by Equation (2).

$$V_{OUT(OVP)} = \frac{V_{OUT(NORMAL)}}{V_{CC(NORMAL)}} \times 27.7 \text{ V} \quad (2)$$

where,

V_{OUT(NORMAL)}: Output voltage in normal operation
 V_{CC(NORMAL)}: VCC pin voltage in normal operation

1.11. Overload Protection (OLP)

When the peak drain current of I_D is limited by Overcurrent Protection operation for a certain time (delay time, t_{DLY}), the IC stops switching operation in the latched mode. This reduces the stress applied on components such as power MOSFETs and secondary diodes.

Figure 1-20 shows the secondary output characteristics in OCP operation.

Figure 1-21 shows the peripheral circuit of FB pin and SS/OLP pin, and Figure 1-22 shows the timing chart in OLP operation.

When the peak drain current of I_D is limited by the Overcurrent Protection (OCP) operation, the output voltage, V_{OUT}, decreases and the feedback current, I_{FB}, from the secondary optocoupler becomes zero. When the OCP operates, the C3 is charged by I_{SSOLP(OLP)} = -11 μA (typ.) that flows from the SS/OLP pin, and the SS/OLP pin voltage starts to increase. When the SS/OLP pin voltage reaches V_{SSOLP(OLP)} = 4.9 V (typ.), the IC stops switching operation in the latched mode.

The approximate delay time, t_{DLY}, is calculated by Equation(3).

$$t_{DLY} \approx \frac{C3 \times \Delta V}{I_{SSOLP(OLP)}} \quad (3)$$

where,

ΔV is the charging voltage of C3 of about 4.9 V

I_{SSOLP(OLP)} has the characteristic of voltage dependence of the SS/OLP pin. When the SS/OLP pin voltage increases, I_{SSOLP(OLP)} decreases. Therefore, the delay time should be considered in the actual operation because Equation (3) and the measured value do not match.

At the power supply startup, the time delay, t_{DLY}, needs to be set longer than the output rise time. When it is short, the OLP operates earlier, resulting in a startup failure.

When the VCC voltage decreases to V_{CC(OFF)} or lower before the C3 voltage reaches 4.9 V by the balance between the voltage decrease rate of C2 of VCC pin and the voltage increase rate of C3, the IC does not turn off in latched mode and intermittently oscillates. Therefore, please pay attention to the delay time setting.

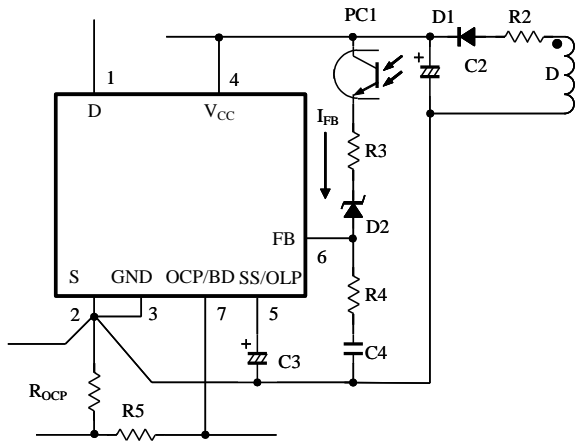


Table 1-1 Reference: OLP Delay Time
 (calculated value in Equation (3) when $\Delta V = 4.9 \text{ V}$,
 $I_{SSOLP(OLP)} = -11 \mu\text{A}$)

Capacitance of C3	t_{DLY}
0.47 μF	209 ms
1 μF	445 ms
2.2 μF	980 ms
3.3 μF	1470 ms
4.7 μF	2094 ms

Figure 1-21. Peripheral Circuit of FB Pin and SS/OLP Pin

 


Figure 1-22. Timing Chart in Overload

switches non-conductive at the upper limit voltage of the range of 100V AC, and switches conductive at the lower limit voltage of the range of 230V AC.

When the negative voltage of the auxiliary winding D is -18 V , the Zener voltage of D6 is about 16 V , and R7 is about $10\text{ k}\Omega$ to $22\text{ k}\Omega$. The constant of D6 and R7 is adjusted by confirming the actual operation.

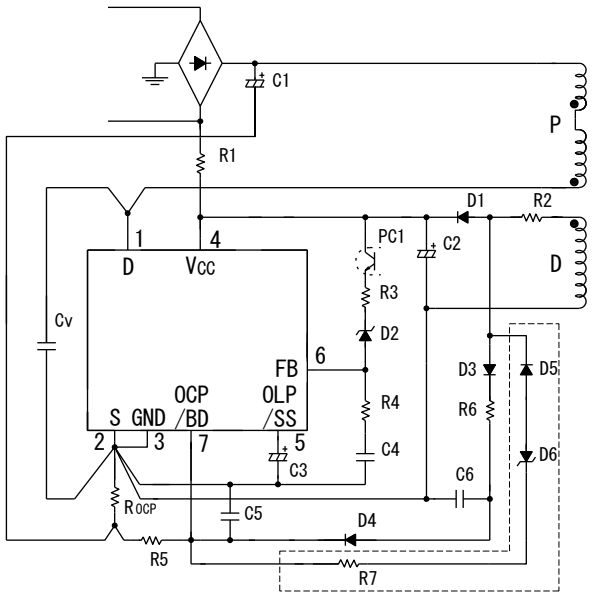


Figure 1-26. Input Voltage Compensation Circuit of OCP

2. Design Notes

2.1. External Components

Take care to use properly rated, including derating as necessary and proper type of components.

- Input and Output Electrolytic Capacitor**
 Apply proper derating to ripple current, voltage, and temperature rise. Use of high ripple current and low impedance types, designed for switch mode power supplies, is recommended.
- Current Detection Resistor, R_{OCP}**
 A high frequency switching current flows to R_{OCP} , and may cause poor operation if a high inductance resistor is used. Choose a low inductance and high surge-tolerant type.

- Peripheral Circuit of Secondary Side Shunt Regulator**

Figure 2-1 shows the secondary side detection circuit with the standard shunt regulator IC.

C8 is for phase compensation. The value of C8 is recommended to be around $0.047\text{ }\mu\text{F}$ to $0.22\text{ }\mu\text{F}$

respectively. They should be selected based on actual operation in the application.

 


Figure 2-1. Peripheral Circuit of Secondary Side Shunt Regulator

- FB Pin Peripheral Circuit**

Figure 2-2 shows the FB pin peripheral circuit. C4 is for high frequency noise reduction and phase compensation.

The recommended value of C4 and R4 are $0.047\text{ }\mu\text{F}$ to $0.22\text{ }\mu\text{F}$, and about $1\text{ k}\Omega$.

C4 and R4 should be connected close to these pins, and are should be selected based on actual operation in the application.

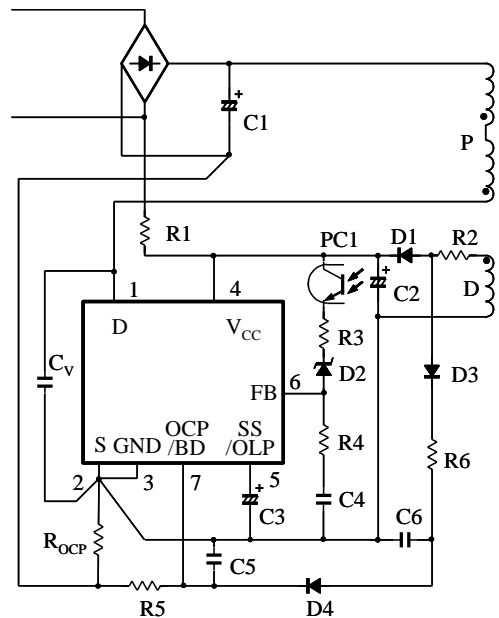


Figure 2-2. FB Pin Peripheral Circuit

- Transformer**

Apply proper design margin to core temperature rise by core loss and copper loss.

Because the switching currents contain high frequency currents, the skin effect may become a consideration. Choose a suitable wire gauge in consideration of the RMS current and a current density of 4 to 6 A/mm². If measures to further reduce temperature are still necessary, the following should be considered to increase the total surface area of the wiring:

- Increase the number of wires in parallel.
- Use litz wires.
- Thicken the wire gauge.

In the following cases, the surge of VCC pin voltage becomes high.

- The surge voltage of primary main winding, P, is high (low output voltage and high output current power supply designs)
- The winding structure of auxiliary winding, D, is susceptible to the noise of winding P.

When the surge voltage of winding D is high, the VCC pin voltage increases and the Overvoltage Protection function (OVP) may be activated. In transformer design, the following should be considered;


The coupling of the winding P and the secondary output winding S should be maximized to reduce the leakage inductance.

- The coupling of the winding D and the winding S should be maximized.
- The coupling of the winding D and the winding P should be minimized.


In the case of multi-output power supply, the coupling of the secondary-side stabilized output winding, S1, and the others (S2, S3...) should be maximized to improve the line-regulation of those outputs.

Figure2-3 shows the winding structural examples of two outputs.

- Winding structural example (a):
S1 is sandwiched between P1 and P2 to maximize the coupling of them for surge reduction of P1 and P2. D is placed far from P1 and P2 to minimize the coupling to the primary for the surge reduction of D.
- Winding structural example (b)
P1 and P2 are placed close to S1 to maximize the coupling of S1 for surge reduction of P1 and P2. D and S2 are sandwiched by S1 to maximize the coupling of D and S1, and that of S1 and S2. This structure reduces the surge of D, and improves the line-regulation of outputs.

 

Winding structural example (a)

 

Winding structural example (b)

Figure2-3. Winding Structural Examples

2.2. Transformer Design

The design of the transformer is fundamentally the same as the power transformer of a Ringing Choke Converter (RCC) system: a self-excitation type flyback converter. However, because the duty cycle will change due to the quasi-resonant operations delaying the turn-on, the duty cycle needs to be compensated.

Figure 2-4 shows the quasi-resonant circuit.

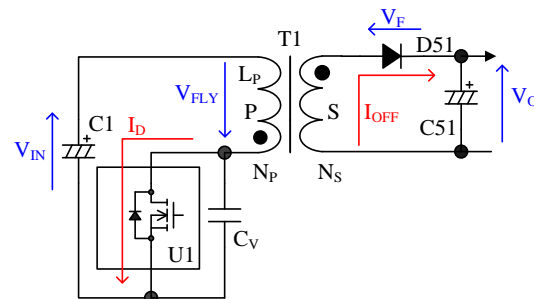


Figure 2-4 Quasi-resonant Circuit

The flyback voltage, V_{FLY} , is calculated as follows:

$$V_{FLY} = \frac{N_P}{N_S} \times (V_O + V_F) \tag{4}$$

where,

- N_P : Primary side number of turns
- N_S : Secondary side number of turns
- V_O : Output voltage
- V_F : Forward voltage drop of D51

The on duty, D_{ON} , at the minimum AC input voltage is calculated as follows:

$$D_{ON} = \frac{V_{FLY}}{V_{IN(MIN)} + V_{FLY}} \quad (5)$$

where,

$V_{IN(MIN)}$: C1 voltage at the minimum AC input voltage
 V_{FLY} : Flyback voltage.

The inductance, L_P' on the primary side, taking into consideration the delay time, is calculated using Equation (6).

$$L_P' = \frac{(V_{IN(MIN)} \times D_{ON})^2}{\left(\sqrt{\frac{2P_O \times f_{MIN}}{\eta_1}} + V_{IN(MIN)} \times D_{ON} \times f_{MIN} \times \pi \sqrt{C_V} \right)^2} \quad (6)$$

where,

$V_{IN(MIN)}$: C1 voltage at the minimum AC input voltage

D_{ON} : On-duty at the minimum input voltage

P_O : maximum output power

f_{MIN} : minimum operation frequency

η_1 : transformer efficiency

C_V : the voltage resonance capacitor connected between the drain and source of the power MOSFET

Each parameter, such as the peak drain current, I_{DP} , is calculated by the following formulas:

$$t_{ONDLY} = \pi \sqrt{L_P' \times C_V} \quad (7)$$

$$D_{ON}' = D_{ON} (1 - f_{MIN} \times t_{ONDLY}) \quad (8)$$

$$I_{IN} = \frac{P_O}{\eta_2} \times \frac{1}{V_{IN(MIN)}} \quad (9)$$

$$I_{DP} = \frac{2 \times I_{IN}}{D_{ON}'} \quad (10)$$

$$N_P = \sqrt{\frac{L_P'}{Al\text{-value}}} \quad (11)$$

$$N_S = \frac{N_P \times (V_O + V_F)}{V_{FLY}} \quad (12)$$

where,

t_{ONDLY} : Delay time of quasi-resonant operation

I_{IN} : Average input current

η_2 : conversion efficiency of the power supply

I_{DP} : peak drain current

D_{ON}' : On-duty after compensation

V_O : Secondary side output voltage

The minimum operation frequency, f_{MIN} , can be calculated by the Equation (14):

$$f_{MIN} = \left[\frac{-\sqrt{\frac{2P_O}{\eta_1}} + \sqrt{\frac{2P_O}{\eta_1} + \frac{4\pi(V_{IN(MIN)} \times D_{ON})^2 \times \sqrt{C_V}}{\sqrt{L_P'}}}}{2\pi \sqrt{C_V} \times V_{IN(MIN)} \times D_{ON}} \right]^2 \quad (13)$$

Figure 2-5 shows the Example of NI-Limit versus AL-Value characteristics.

Choose the ferrite core that does not saturate and provides a design margin in consideration of temperature effects and other variations to NI-Limit versus AL-Value characteristics.

Al-value is calculated by using L_P' and N_P . NI is calculated by using Equation (14).

It is recommended that Al-value and NI provide the design margin of 30 % or more for saturation curve of core.

$$NI = N_P \times I_{DP} \quad (AT) \quad (14)$$

where,

N_P : Primary side number of turns

I_{DP} : Peak switching current

 


Figure 2-5. Example of NI-Limit versus AL-Value characteristics

2.3. PCB Trace Layout and Component Placement

Since the PCB circuit trace design and the component layout significantly affects operation, EMI noise, and power dissipation, the high frequency PCB trace should be low impedance with small loop and wide trace.

In addition, the ground traces affect radiated EMI noise, and wide, short traces should be taken into account.

Figure 2-6 shows the circuit design example.

(1) Main Circuit Trace Layout

This is the main trace containing switching currents, and thus it should be as wide trace and small loop as possible.

If C1 and the IC are distant from each other, placing a capacitor such as film capacitor (about 0.1 μF and with proper voltage rating) close to the transformer or the IC is recommended to reduce impedance of the high frequency current loop.

(2) Control Ground Trace Layout

Since the operation of IC may be affected from the large current of the main trace that flows in control ground trace, the control ground trace should be separated from main trace and connected as close to the R_{OCP} pin as possible.

(3) VCC Trace Layout

This is the trace for supplying power to the IC, and thus it should be as small loop as possible. If C3 and the IC are distant from each other, placing a capacitor such as film capacitor C_f (about 0.1 μF to

1.0 μF) close to the VCC pin and the GND pin is recommended.

(4) R_{OCP} Trace Layout

R_{OCP} should be placed as close as possible to the S pin and GND pin. The C1 negative trace and the R5 trace should be close to the base of R_{OCP} to prevent the common impedance or the switching current from affecting the control circuit.

(5) Peripheral components of the IC

The components for control connected to the IC should be placed as close as possible to the IC, and should be connected as short as possible to the each pin.

(6) Secondary Rectifier Smoothing Circuit Trace Layout:

This is the trace of the rectifier smoothing loop, carrying the switching current, and thus it should be as wide trace and small loop as possible. If this trace is thin and long, inductance resulting from the loop may increase surge voltage at turning off the power MOSFET. Proper rectifier smoothing trace layout helps to increase margin against the power MOSFET breakdown voltage, and reduces stress on the clamp snubber circuit and losses in it.

(7) Thermal Considerations

Because the power MOSFET has a positive thermal coefficient of R_{DS(ON)}, please pay attention to the thermal design.

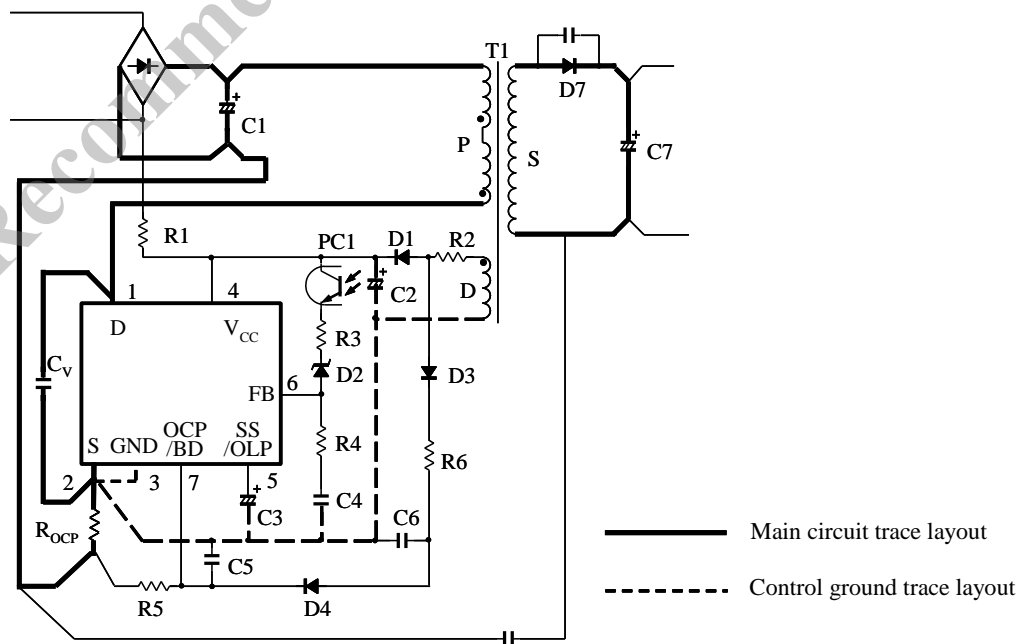


Figure 2-6. Peripheral Circuit Example

Important Notes

- All data, illustrations, graphs, tables and any other information included in this document as to Sanken's products listed herein (the "Sanken Products") are current as of the date this document is issued. All contents in this document are subject to any change without notice due to improvement of the Sanken Products, etc. Please make sure to confirm with a Sanken sales representative that the contents set forth in this document reflect the latest revisions before use.
- The Sanken Products are intended for use as components of general purpose electronic equipment or apparatus (such as home appliances, office equipment, telecommunication equipment, measuring equipment, etc.). Prior to use of the Sanken Products, please put your signature, or affix your name and seal, on the specification documents of the Sanken Products and return them to Sanken. When considering use of the Sanken Products for any applications that require higher reliability (such as transportation equipment and its control systems, traffic signal control systems or equipment, disaster/crime alarm systems, various safety devices, etc.), you must contact a Sanken sales representative to discuss the suitability of such use and put your signature, or affix your name and seal, on the specification documents of the Sanken Products and return them to Sanken, prior to the use of the Sanken Products. The Sanken Products are not intended for use in any applications that require extremely high reliability such as: aerospace equipment; nuclear power control systems; and medical equipment or systems, whose failure or malfunction may result in death or serious injury to people, i.e., medical devices in Class III or a higher class as defined by relevant laws of Japan (collectively, the "Specific Applications"). Sanken assumes no liability or responsibility whatsoever for any and all damages and losses that may be suffered by you, users or any third party, resulting from the use of the Sanken Products in the Specific Applications or in manner not in compliance with the instructions set forth herein.
- In the event of using the Sanken Products by either (i) combining other products or materials therewith or (ii) physically, chemically or otherwise processing or treating the same, you must duly consider all possible risks that may result from all such uses in advance and proceed therewith at your own responsibility.
- Although Sanken is making efforts to enhance the quality and reliability of its products, it is impossible to completely avoid the occurrence of any failure or defect in semiconductor products at a certain rate. You must take, at your own responsibility, preventative measures including using a sufficient safety design and confirming safety of any equipment or systems in/for which the Sanken Products are used, upon due consideration of a failure occurrence rate or derating, etc., in order not to cause any human injury or death, fire accident or social harm which may result from any failure or malfunction of the Sanken Products. Please refer to the relevant specification documents and Sanken's official website in relation to derating.
- No anti-radioactive ray design has been adopted for the Sanken Products.
- No contents in this document can be transcribed or copied without Sanken's prior written consent.
- The circuit constant, operation examples, circuit examples, pattern layout examples, design examples, recommended examples, all information and evaluation results based thereon, etc., described in this document are presented for the sole purpose of reference of use of the Sanken Products and Sanken assumes no responsibility whatsoever for any and all damages and losses that may be suffered by you, users or any third party, or any possible infringement of any and all property rights including intellectual property rights and any other rights of you, users or any third party, resulting from the foregoing.
- All technical information described in this document (the "Technical Information") is presented for the sole purpose of reference of use of the Sanken Products and no license, express, implied or otherwise, is granted hereby under any intellectual property rights or any other rights of Sanken.
- Unless otherwise agreed in writing between Sanken and you, Sanken makes no warranty of any kind, whether express or implied, including, without limitation, any warranty (i) as to the quality or performance of the Sanken Products (such as implied warranty of merchantability, or implied warranty of fitness for a particular purpose or special environment), (ii) that any Sanken Product is delivered free of claims of third parties by way of infringement or the like, (iii) that may arise from course of performance, course of dealing or usage of trade, and (iv) as to any information contained in this document (including its accuracy, usefulness, or reliability).
- In the event of using the Sanken Products, you must use the same after carefully examining all applicable environmental laws and regulations that regulate the inclusion or use of any particular controlled substances, including, but not limited to, the EU RoHS Directive, so as to be in strict compliance with such applicable laws and regulations.
- You must not use the Sanken Products or the Technical Information for the purpose of any military applications or use, including but not limited to the development of weapons of mass destruction. In the event of exporting the Sanken Products or the Technical Information, or providing them for non-residents, you must comply with all applicable export control laws and regulations in each country including the U.S. Export Administration Regulations (EAR) and the Foreign Exchange and Foreign Trade Act of Japan, and follow the procedures required by such applicable laws and regulations.
- Sanken assumes no responsibility for any troubles, which may occur during the transportation of the Sanken Products including the falling thereof, out of Sanken's distribution network.
- Although Sanken has prepared this document with its due care to pursue the accuracy thereof, Sanken does not warrant that it is error free and Sanken assumes no liability whatsoever for any and all damages and losses which may be suffered by you resulting from any possible errors or omissions in connection with the contents included herein.
- Please refer to the relevant specification documents in relation to particular precautions when using the Sanken Products, and refer to our official website in relation to general instructions and directions for using the Sanken Products.
- All rights and title in and to any specific trademark or tradename belong to Sanken or such original right holder(s).

DSGN-CEZ-16002